

Light Bulb Paper Circuit

Materials

Copper tape

LED Light Emitting Diodes Bulb

CR2032 3V Lithium Battery

Scissors

Tissue paper (for gift bags)

Sharpie

Tape

Ribbon

- Follow the directions on the video.
 - Be sure to line your copper tape so that the bulb is where you would like it to shine through the tissue paper.
 - Be sure that the copper tape is pressed down tight, and the circuit is closed completely.
 - Place the battery face up with the side with letters on the paper. Be sure it is behind the outlet drawing when folded.
-

Print and cut



